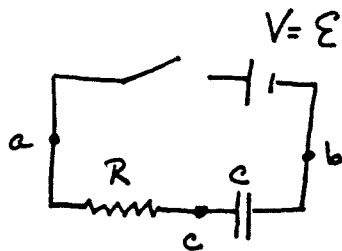


R-C Circuit



When switch is thrown current begins to flow through ckt, capacitor charges up creating p.d. V_{cb} decreasing p.d. V_{ac} [$V = V_{ac} + V_{cb}$] thus decreasing the current $V_{ac} = iR$. At any instant

$$V_{ac} = iR \quad V_{cb} = \frac{q}{C}$$

$$V_{ab} = V = iR + \frac{q}{C} \quad \text{Solving for the}$$

$$\text{current } i = \frac{V}{R} - \frac{q}{RC}$$

at $t=0$ $q=0$ $i = I_0 = \frac{V}{R}$ as ①

charge increases current decreases until finally drops to zero $q \rightarrow Q$ $Q = CV$ ②

To find out what happens between ① + ② must do some math. Recall def'n of current

$$i = \frac{dq}{dt} = \frac{V}{R} - \frac{q}{RC}$$

which we rearrange to get all charge on one side of eqn

$$\frac{dq}{dt} = \frac{VC - q}{RC}$$

$$\frac{dq}{VC - q} = \frac{dt}{RC}$$

$$\int \frac{dq}{VC - q} = \frac{1}{RC} \int dt$$

Integrating

$$\int \frac{1}{q} = \ln q \quad \int \frac{dq}{c - q} = -\ln(c - q)$$

$$-\ln(VC - q) = \frac{t}{RC} + \text{const}$$

$$t=0 \quad q=0 \quad \text{Thus}$$

$$\text{const} = -\ln(VC)$$

$$\ln(VC - q) - \ln VC = -\frac{t}{RC}$$

$$\ln\left(\frac{VC - q}{VC}\right) = -\frac{t}{RC}$$

Exponentiating

$$e^{\left(\ln \frac{VC - q}{VC}\right)} = \frac{VC - q}{VC} = 1 - \frac{q}{VC}$$

$$1 - \frac{q}{VC} = e^{-t/RC}$$

Rearranging


$$q = VC(1 - e^{-t/RC}) = Q(1 - e^{-t/RC})$$

$$i = \frac{dq}{dt} = \frac{d}{dt} (VC - VCe^{-t/RC})$$


Differentiating

$$\frac{d}{dt} (e^{-t/RC}) = -\frac{e^{-t/RC}}{RC}$$
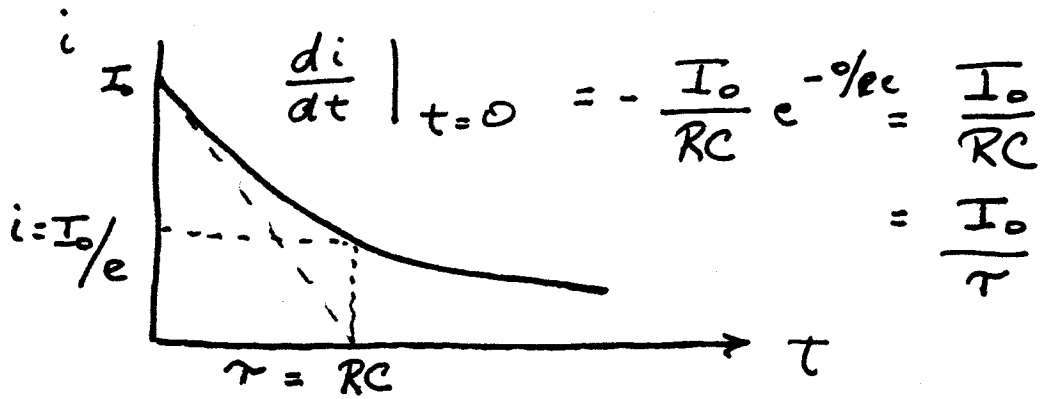
$$i = \frac{V}{R} e^{-t/RC} = I_0 e^{-t/RC}$$




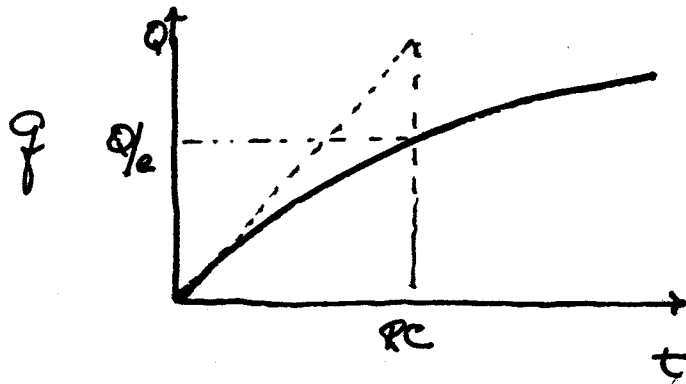Initially current decreasing as $\frac{I_0}{\tau}$. If continued to decrease at that rate. $I=0$ at $t = \tau = RC$. In real life when $t = \tau$ $i = I_0/e = \frac{I_0}{2.7182818285}$



$V_{cb} = \frac{q}{C}$
So capacitor voltage looks like this too

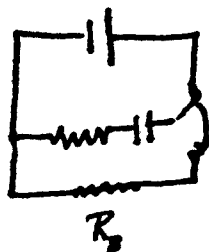$\tau = RC$ is time constant or "relaxation time" of circuit. This is how automobile turn signals work. Filament of bulb = R_3 , place capacitance in series



Also Christmas tree lights, etc

When v_{bc} reaches some value (det'd by time constant of circuit) switch is activated discharging through lamp - light flashes!

Discharging capacitor, now $V_{ab} = 0$

$$0 = v_{ac} + v_{cb}$$

$$i = \frac{q}{RC}$$

$$t=0 \quad q = Q \quad I_0 = \frac{V_0}{R} = \frac{Q_0}{RC}$$

$$i = I_0 e^{-t/RC}$$

$$q = Q_0 e^{-t/RC}$$

— 0 —

How do we measure current, voltage resistance? Not necessarily a simple matter, esp. if we want to make measurement w/ high accuracy because placing instrument in circuit introduces its own characteristics alters circuit