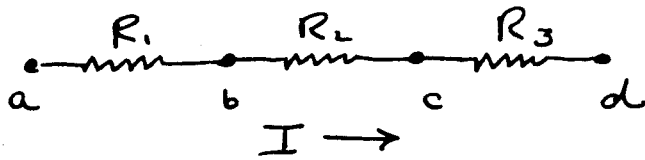


Complex DC Circuits

Resistors in series:



Same current in each resistor

$$V_{ab} = IR_1$$

$$V_{bc} = IR_2$$

$$V_{cd} = IR_3$$


$$\begin{aligned} V_{ad} &= \text{potential difference across network} \\ &= V_{ab} + V_{bc} + V_{cd} = IR_1 + IR_2 + IR_3 \\ &= I(R_1 + R_2 + R_3) \end{aligned}$$

What is the equivalent resistance such that we can write

$$V_{ad} = I \cdot R_{eq} \quad \text{or} \quad R_{eq} = \frac{V_{ad}}{I}$$

$$V_{ad} = I R_{eq} = I (R_1 + R_2 + R_3)$$

$$R_{eq} = R_1 + R_2 + R_3$$

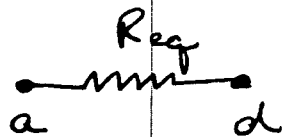


Series resistor

$$R_{eq} = \sum R_i$$

$R_{eq} >$ any R in ckt

Resistors in parallel

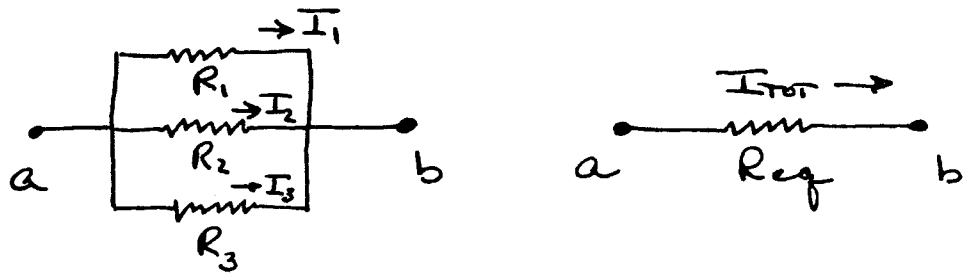

Potential difference V_{ab} is the same regardless of path

$$V_{ab} = I_1 R_1 = I_2 R_2 = I_3 R_3$$

Total current $a \rightarrow b$

$$I_{TOT} = I_1 + I_2 + I_3$$

$$I_1 = \frac{V_{ab}}{R_1} \quad I_2 = \frac{V_{ab}}{R_2} \quad I_3 = \frac{V_{ab}}{R_3}$$

$$I_{TOT} = \frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2} + \frac{V_{ab}}{R_3} = V_{ab} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$I_{TOT} = \frac{V_{ab}}{R_{eq}} \quad \text{Ohm's Law}$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Parallel resistors



$$\boxed{\frac{1}{R_{eq}} = \sum \frac{1}{R_i}}$$

5 track System

Power Amplifier 150 Watts per channel

Speakers usually 4Ω or 8Ω

In series

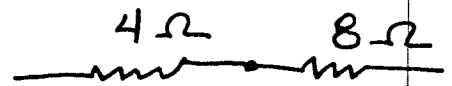
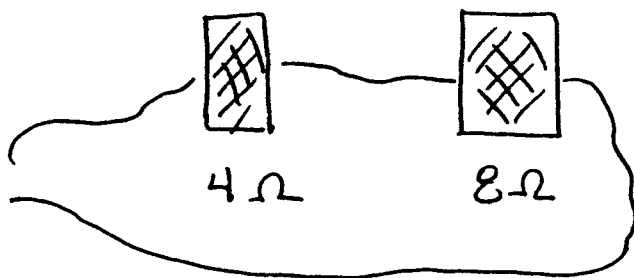


$$R_{eq} = 4 \Omega + 8 \Omega \\ = 12 \Omega$$

$$P = I^2 R \quad I = \left(\frac{P}{R} \right)^{1/2} = \sqrt{\frac{150 W}{12 \Omega}}$$

$$\underline{I = 3.5 A}$$

Parallel

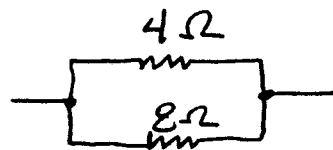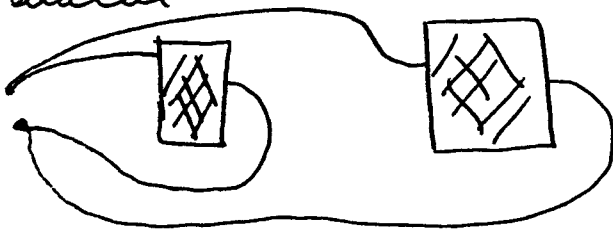

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \\ = \frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2} \\ = \frac{R_1 + R_2}{R_1 R_2}$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{32 \Omega^2}{12 \Omega}$$

Some transistor amps don't like $R < 4 \Omega$ cause of large currents

$$R_{eq} = \underline{2.67 \Omega}$$

note this is lower than either ind. resists

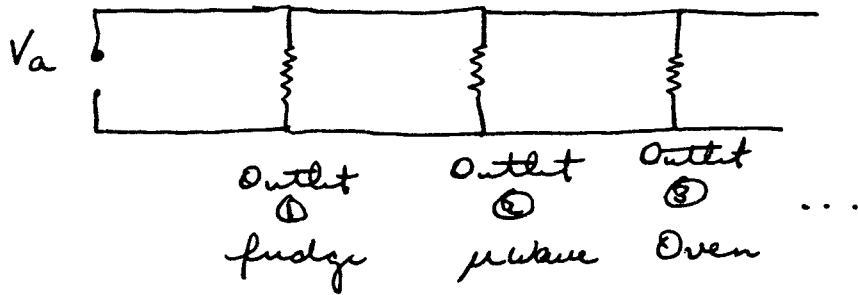Household wiring - lights, appliances
is usually parallel




Don't load up too much; as you add
add'l parallel resistances the R_{eq} goes
down I goes up, trips circuit breaker
(e.g. 15A) or worse...

ex

What is I

I_1, I_2, I_3

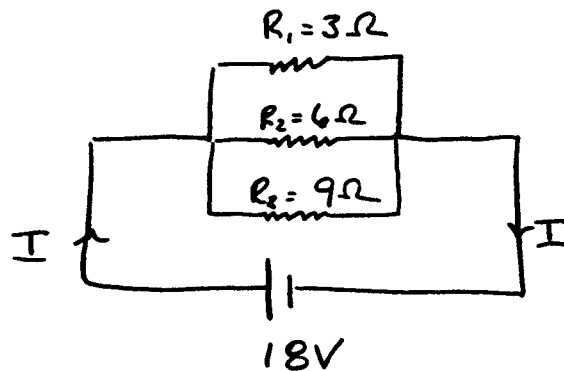

$V = 18V$ across each resistor

$$I_1 = \frac{V}{R_1} = \frac{18V}{3\Omega} = 6A$$

$$I_2 = \frac{18V}{6\Omega} = 3A$$

$$I_3 = \frac{18V}{9\Omega} = 2A$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{3\Omega} + \frac{1}{6\Omega} + \frac{1}{9\Omega} = \frac{11}{18\Omega}$$

$$R_{eq} = \frac{18}{11}\Omega \quad I = \frac{V}{R_{eq}} = \frac{18}{18/11} = 11 \text{ Amp} = I_1 + I_2 + I_3$$