

BATTERIES - ELECTROMOTIVE

A battery is a SOURCE of potential difference (It can be thought of as a way of carrying charge uphill)

~1V Remember the toy POTATO BATTERY using
Zn Cu a strip of copper, a strip of zinc + a potato?

Almost any two metals placed in a common electrolyte usually acid solution will create a p.d. depending upon the ease with which the metal gives up or takes on an electron

ELECTROMOTIVE SERIES


Li	LITHIUM	- 3.0 V
K	POTASSIUM	- 2.9 V
Zn	ZINC	- 0.76
Cd	CADMIUM	- 0.40
Ni	NICKEL	- 0.25
Pb	LEAD	- 0.13
Cu	COPPER	+ 0.34
Ag	SILVER	+ 0.8
Au	GOLD	+ 1.3

ACCEPTS
e⁻

DO NOT
ACCEPT
e⁻


EMF

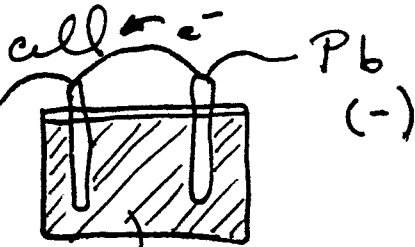Up until this time we have introduced sources of potential difference w/o being concerned about the characteristics of the "source" itself. Let's consider an automobile battery - lead-acid storage cell




H_2SO_4

1) at negative electrode

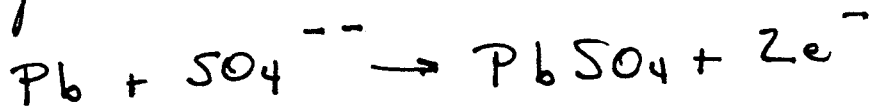


2) at the positive electrode

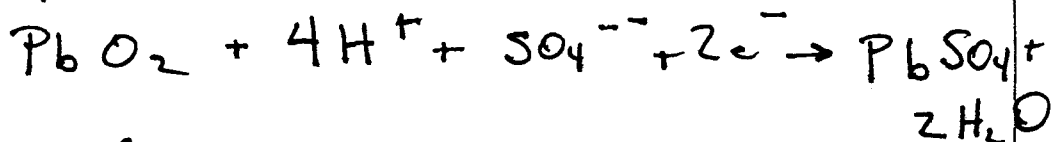

Overall




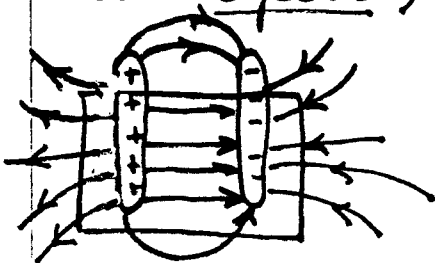When the cell is isolated w/o anything connecting terminals (we say the circuit is open) it still maintains one



terminal at a higher electric potential (the + terminal) than the other terminal (the - terminal)

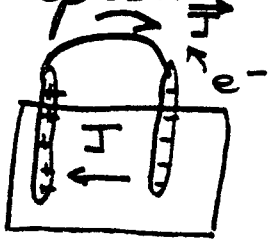If we add a connecting wire charge flows around the circuit and a current is established.



Inside the cell + charge is transported from the - terminal to the + terminal and vice versa. These

directions of charge transport are opposite to the way that charges would flow on purely electrical grounds. In

the absence of connection between pos + neg terminals charges do not move implying that $\nabla \cdot \vec{E}$ is counteracting

the electrostatic force or an "equivalent" non-electrostatic field

$$\vec{E} = \vec{E}_n + \vec{E}_e = 0 \quad \vec{E}_n = -\vec{E}_e$$


$$\oint E_{||} ds = 0$$

$$\oint_{\text{cell}} E_{||} ds = \int E_R dl = V_{ab} = \mathcal{E}$$

work performed

" ELECTRO MOTIVE POTENTIAL

charges in sol'n to flow

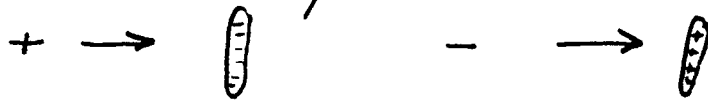


net chg on terminals would be neutralized $\Rightarrow V_{ab} \rightarrow 0$. In this case

$$\mathcal{E} = V_{ab}$$

OPEN CIRCUIT

CLOSED CIRCUIT

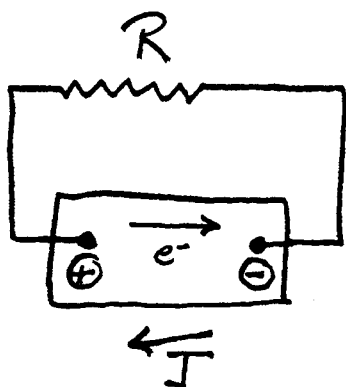Internal resistance \Rightarrow chgs do not flow fully through source. To maintain V_{ab} must maintain chg. on terminals, chgs must flow through source. Source must perform work to move electrons from



$$V_{ab} = \mathcal{E} - Ir = IR$$


$$I = \frac{\mathcal{E}}{R+r}$$

current in source from - to +

In general for any number of sources, resistances internal + external

$$I = \frac{\sum \mathcal{E}}{\sum R}$$

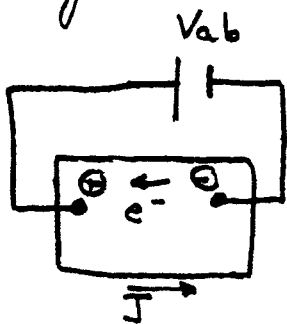
If connected to external circuit containing other sources can possibly get current \vec{J} from + to -



(P.d. applied externally greater than source e.m.f \Rightarrow source charges)

$$V_{ab} = \mathcal{E} + Ir$$

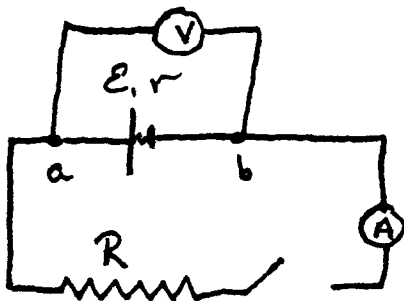Measure current, voltage w/ meters
 (A) (V) ammeter, voltmeter



$$\mathcal{E} = 12V \quad r = 2\Omega$$

$$R = 4\Omega$$

Circuit open

$$V_{ab} = 12V \text{ measured}$$


Switch closed, p.d.

causes current to flow:

$$I = \frac{\mathcal{E}}{R+r} = \frac{12V}{4\Omega + 2\Omega} = 2A$$

$$V_{ab} = IR = 2A \cdot 4\Omega = 8V$$
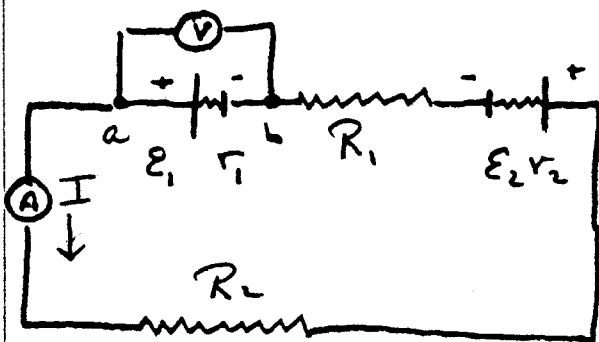
$$= \mathcal{E} - Ir = 12V - 2\Omega \cdot 2A = 8V$$



Must define direction of positive current - can take our pick, but must be consistent. Then emf is positive if non-electrostatic force in direction of current.

\mathcal{E} positive if I from - to +

$$I = \frac{\sum \mathcal{E}}{\sum R} = \frac{\mathcal{E}_1 - \mathcal{E}_2}{r_1 + r_2 + R_1 + R_2}$$

measured by ammeter

$$V_{ab} = \mathcal{E}_1 - I r_1 = I (R_1 + r_2 + R_2)$$

p.d. across source 1
p.d. across remainder of circuit

measured by voltmeter
emf

Car battery: 12 V causes current I to flow through system when ignition turned on performs work starting car

$$V_{ab} = \mathcal{E} - I r = 12V - I$$

car engine runs generate (alternate)

which generates $V_{ab} > 12 \text{ V}$

$$V_{ab} = \mathcal{E} + Ir$$

recharges car battery. What happens when car battery goes dead?

\mathcal{E} relatively const but $r \rightarrow$ up battery won't charge. If you take a battery in to svc. station they check voltage on open circuit


$V_{ab} = \underline{\underline{\mathcal{E}}}$ checking emf then test "under load"

$$V_{ab} = \mathcal{E} - Ir \text{ checking } r$$

Car hard to start when cold due to $r = r(T)$ such that r high when T low.

WORK AND POWER

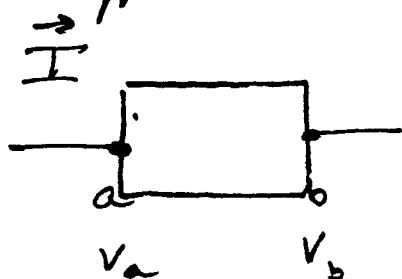V_{ab} recall is potential energy difference per unit charge, thus if we move charge ΔQ through p.d. V_{ab} we have performed work



$$\Delta W = \Delta E_p = \Delta Q (V_a - V_b)$$

If we have current $I = \frac{\Delta Q}{\Delta t}$

$$\Delta Q = I \Delta t$$

$$\Delta W = V_{ab} I \Delta t$$

Source of p.d. transfers energy to circuit between a and b at a rate

$$P = \frac{\Delta W}{\Delta t} = \frac{V_{ab} I \cancel{\Delta t}}{\cancel{\Delta t}}$$

$$\boxed{P = VI} \quad \text{Power}$$

If $V_a > V_b$ energy transferred into circuit

$V_b > V_a$ charge gains energy at expense of some other form in circuit

$$P = V \cdot I$$
$$1 \text{ WATT} = (1\text{V})(1\text{A}) = (1\text{J C}^{-1})(1\text{C s}^{-1}) = 1\text{J s}^{-1} = 1\text{W}$$

100 W light bulb - power rating is rate of power consumption of bulb (unfortunately not rate of output of radiant energy). 115 V household voltage \Rightarrow

$$100\text{W} = 115\text{V} \cdot I$$

$$I = \frac{100\text{W}}{115\text{V}} = 0.87\text{A}$$

current flowing.