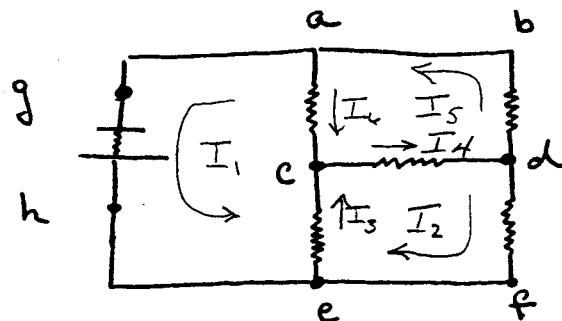


KIRCHOFF'S RULES

Not all networks can be reduced to simple series-parallel combinations

e.g.



We use the method described by Kirchoff's rules to solve such networks

Definitions

- 1) Branch Point - point where 3 or more conductors meet

Branch points alone: a, c, d, e


- 2) Loop - any closed conducting path
Closed loops:

a b d c a, c d f e c, g h e c a g,
g h e f d b a g, a b d f e c a,
etc.

2) Use the point rule to reduce the unknown currents. If there are n branch points, apply the point rule to $n-1$ points (last one is not independent)

Above ekt:


a

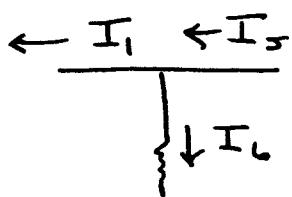

$$I_s = I_1 + I_6$$


(in) (out)

c

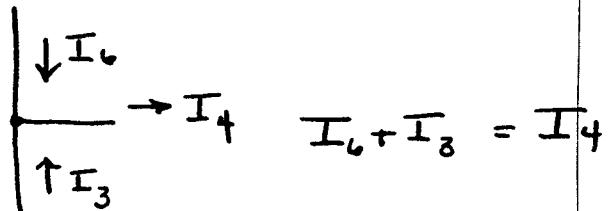


$$I_6 + I_3 = I_4$$

e

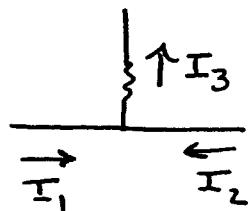

$$I_1 + I_2 = I_3$$

d

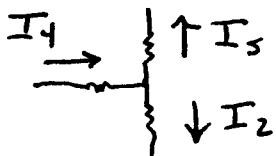


$$I_4 = I_s + I_2$$


This is redundant;
duplicate info
need only 3


3) Separate the circuit into individual closed loops. Choose a closed loop and a direction to proceed around the loop. Apply the loop rule in the chosen direction adding emfs and IR terms as follows:

emf is positive if from - to +
negative " " + to -

IR term positive if same direction as current
negative if opposite " "

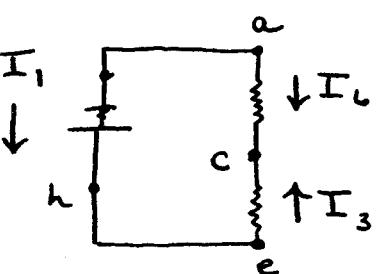
1)  Proceed ccw $\sum E = \sum IR$
 $E = I_1 r + I_3 R - I_6 R$

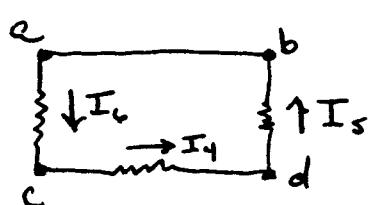2)  CCW, no E
 $\Theta = I_6 R + I_4 R + I_5 R$

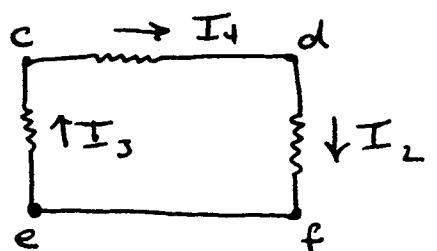3)  CW
 $\Theta = I_3 R + I_4 R + I_2 R$

- 4) Use as many loops as needed
 5) Solve n eqns simultaneously for n unknowns

EXAMPLE

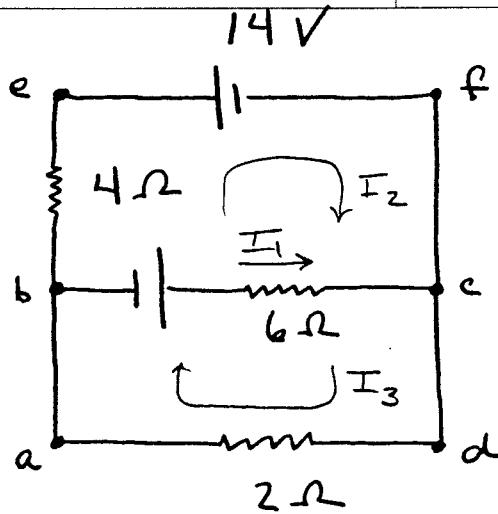

Branch points : b + c


$$\text{Point rule at } c \quad I_1 + I_2 = I_3 \quad \textcircled{1}$$

or

$$I_1 + I_2 - I_3 = 0$$


(note applying point rule at b yields $I_2 = I_1 + I_3$, which is equivalent; 2 branch points \Rightarrow 1 eqn)

Loops abcd a, abefcd a, befcb

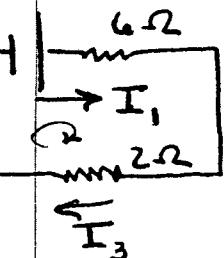

Loop rule abcda proceeding cw
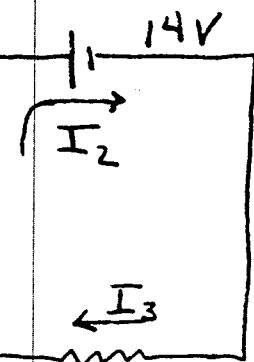
$$10V = I_1 6\Omega + I_3 2\Omega \quad \textcircled{2}$$



Loop rule abefcd a proceeding cw

$$-14V = I_2 4\Omega + I_3 2\Omega \quad \textcircled{3}$$

3eqns 3 unknowns Substitute $\textcircled{1}$ in $\textcircled{2}$

$$10V = I_1 6\Omega + (I_1 + I_2) 2\Omega$$

reduces to $I_2 = 5 - 4I_1$ Substitute in $\textcircled{3}$

$$-14V = (5 - 4I_1) 4\Omega + 2\Omega (I_1 + 5 - 4I_1)$$

$$-14 = 20 - 16I_1 + 2I_1 + 10 - 8I_1$$

Collecting terms

$$22I_1 = 44$$

$$I_1 = 2 \text{ amper}$$


$$I_2 = 5 - 4I_1 = 5 - 8$$

$$= -3 \text{ amper}$$

$$I_3 = I_1 + I_2 = 2 - 3$$

$$= -1 \text{ amp}$$

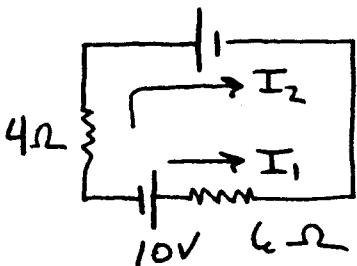Could equally well have used loop bef cb
Proced cw




$$-14V - 10V = -I_1 4\Omega + I_2 4\Omega$$

$$-24 = -4I_1 + 4(5 - 4I_1)$$

$$22I_1 = 44$$



$$I_1 = 2 \text{ amper} \quad \dots$$

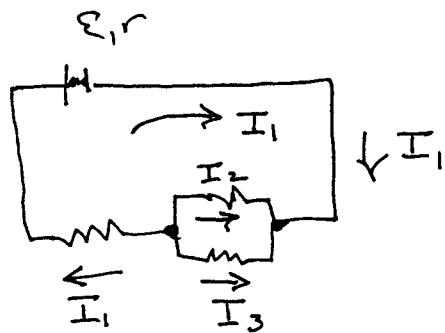Yesterday's
 PROBLEM
 JAMES
 KIRCHOFF'S
 RULES




NODES

a, b are nodes

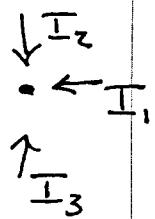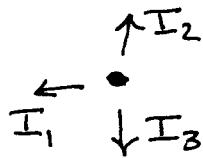

$$0 = -I_1 - I_2 - I_3$$

LOOPS

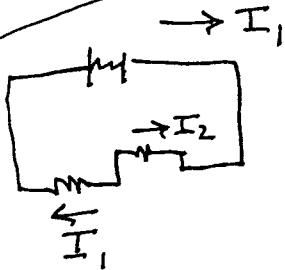

$$\sum \varepsilon = \sum IR$$

CW

$$0 = I_2 R_2 - I_3 R_3$$

$$\text{CCW } \varepsilon = -I_1 r - I_1 R_1 + I_2 R_2$$

$$18V = -I_1 2\Omega - I_1 2\Omega + I_2 6\Omega$$

$$= -I_1 4\Omega + I_2 6\Omega$$

$$\rightarrow I_2 = I_3 \frac{R_3}{R_2} \quad \text{or} \quad I_3 = I_2 \frac{R_2}{R_3}$$

$$\begin{aligned} I_1 &= -I_2 - I_2 \frac{R_2}{R_3} \\ &= -I_2 (1 + \frac{R_2}{R_3}) \end{aligned}$$

$$I_2 = -\frac{I_1}{1 + R_2/R_3} = -\frac{I_1}{1 + 4R_{3,2}}$$

Select

$$18V = -I_1 \cdot 4\Omega + 4\Omega \left(-\frac{I_1}{3} \right)$$

$$\xrightarrow{-I_1 \cdot 4\Omega}$$

$$I_1 = -3A \quad \text{oops } I_1 \text{ goes other way}$$

$$I_2 = -\frac{I_1}{3} = 1A$$

$$I_3 = I_2 \cdot 2 = 2A$$