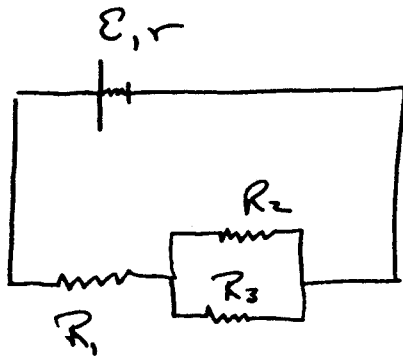


EXAMPLE



$$\mathcal{E} = 18V$$

$$R_1 = 2\Omega$$


$$R_2 = 6\Omega$$

$$R_3 = 3\Omega$$

$$r = 2\Omega$$

What are currents, p.d. in above circuit

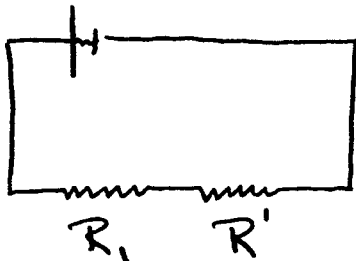1) Replace $R_2 + R_3$ w/ equivalent resistance R'



(PARALLEL)

$$\frac{1}{R'} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{R_2 + R_3}{R_2 R_3}$$


$$R' = \frac{R_2 R_3}{R_2 + R_3}$$

$$R' = \frac{6\Omega \cdot 3\Omega}{6\Omega + 3\Omega}$$

$$= \frac{18\Omega^2}{9\Omega}$$

$$\underline{R' = 2\Omega}$$

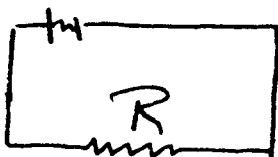2) Can replace $R_1 + R'$ w/ equivalent resistance R



(SERIES)

$$R = R_1 + R' = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$R = R_1 + R' = 2\Omega + 2\Omega$$

$$\underline{R = 4\Omega}$$

$$I = \frac{\Sigma \mathcal{E}}{\Sigma R} = \frac{\mathcal{E}}{R+r}$$

$$= \frac{\mathcal{E}}{r+R_1 + \frac{R_2 R_3}{R_2+R_3}}$$

$$V_1 = I R_1 = \left(\frac{\mathcal{E}}{r+R_1 + \frac{R_2 R_3}{R_2+R_3}} \right) R_1$$

$$V_2 = I R' = V_3$$

$$I_2 = \frac{V_2}{R_2}$$

$$I_3 = \frac{V_3}{R_3}$$

nb $I_2 + I_3 = I$

$$I = \frac{18V}{4\Omega + 2\Omega}$$

$$\underline{I = 3A}$$

$$V_1 = 3A \cdot 2\Omega$$

$$\underline{V_1 = 6V}$$

$$V_2 = 3A \cdot 2\Omega$$

$$V_{2,3} = 6V$$


$$I_2 = \frac{6V}{6\Omega}$$

$$I_2 = 1A$$

$$I_3 = \frac{6V}{3\Omega}$$

$$I_3 = 2A$$

$$I = 2A + 1A = 3A \checkmark$$

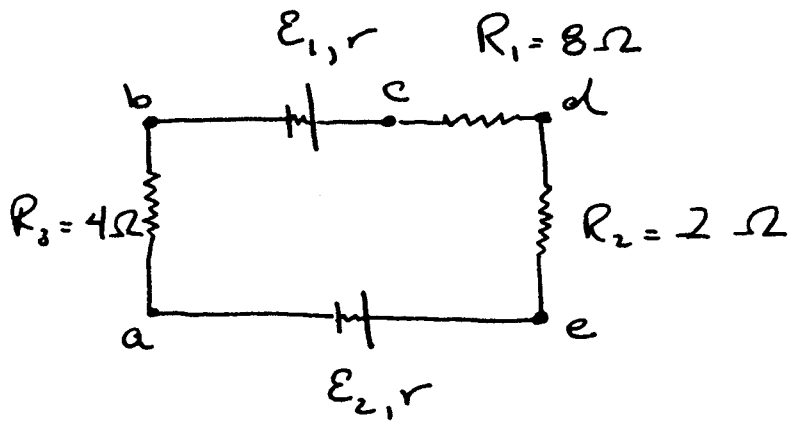

$$\mathcal{E}_1 = 10V \quad \mathcal{E}_2 = 18V \quad r = 1\Omega$$

1) Select (arbitrarily, it's OK) current direction
 In ckt above it's pretty easy to see that
 current will be ccw, but it doesn't
 matter. Assume I cw

2) Apply source rule

$$I = \frac{V}{R} = \frac{\sum \mathcal{E}}{\sum R}$$

with the following convention

\mathcal{E} is positive if I from $-$ to $+$ internally
 \mathcal{E} " negative if I " $+$ to $-$ " "

$$\mathcal{E}_1 = +10V \quad \mathcal{E}_2 = -18V$$


$$I = \frac{10V - 18V}{8\Omega + 2\Omega + 4\Omega + 2 \cdot 1\Omega}$$

$$= - \frac{8V}{16\Omega} = - \frac{1}{2} \text{ Amps} \quad \left(\begin{array}{l} - \text{ sign tells} \\ \text{no current} \\ \text{is opposite dir} \end{array} \right)$$


Look at p.d. a-d

Consider the following common sense rules

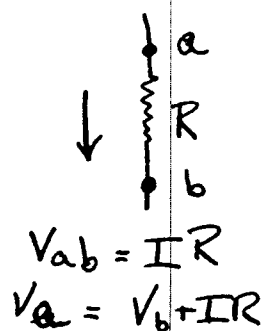1) Potential is higher "upstream" of resistance - resistor dissipates energy thus current has higher energy before resistor



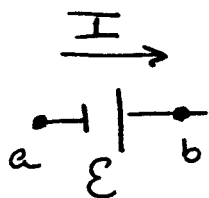2) When current is "with" source of EMF source is "pump" elevating ch to higher potential - Potential is higher "downstream"




$$V_b = V_a + E$$

$$V_{ba} = -V_{ab} = E$$

(n. b. if there is internal resistance a little of the energy gained is lost to dissipation

$$V_{ba} = E - Ir$$

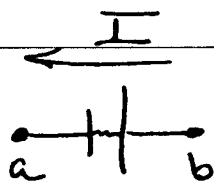3) When current is "against" source work is done against mechanical or chemical "non-electrostatic" force (and also against internal resistance) Energy is higher upstream



$$V_b = V_a + \mathcal{E} + Ir$$

$$V_{ba} = -V_{ab} = \mathcal{E} + Ir$$


[note that potential is always higher at positive terminal of source

$\mathcal{E} - Ir$ current with source

$\mathcal{E} + Ir$ current against source

Now a-b
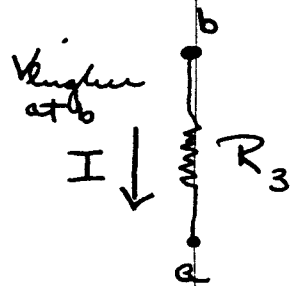
$$V_{ba} = IR_3 = \frac{1}{2} \text{ A} \cdot 4 \Omega = \underline{2V}$$




[remember this is potential at b wrt a $V_{ba} = V_b - V_a = -V_{ab}$]

b is uphill from a

b-c

$$V_{cb} = \mathcal{E}_1 + Ir \quad (\text{since current is against source})$$

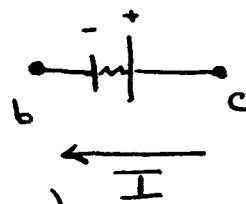
$$= 10V + \frac{1}{2} \text{ A} \cdot 1 \Omega = \underline{10\frac{1}{2} V}$$



c is uphill from b

c-d
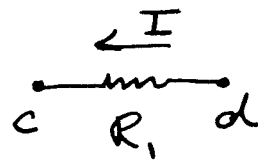
$$V_{dc} = IR_1 = \frac{1}{2} \text{ A} \cdot 8 \Omega = \underline{4V}$$



d is uphill from c

$$V_{da} = V_{dc} + V_{cb} + V_{ba} = 4V + 10\frac{1}{2} V + 2V = \underline{16\frac{1}{2} V}$$